



Sharif University of Technology
Department of Computer Engineering

Digital System Design

Algorithmic State Machine (ASM)

Siavash Bayat-Sarmadi


Introduction

2

- Digital system design
 - ▣ Design of digital circuits performing data-processing operations
 - Arithmetic, logic, etc.
 - ▣ Design of control circuit
 - Determines the sequence of performing above operations

Introduction (Cont.)

3

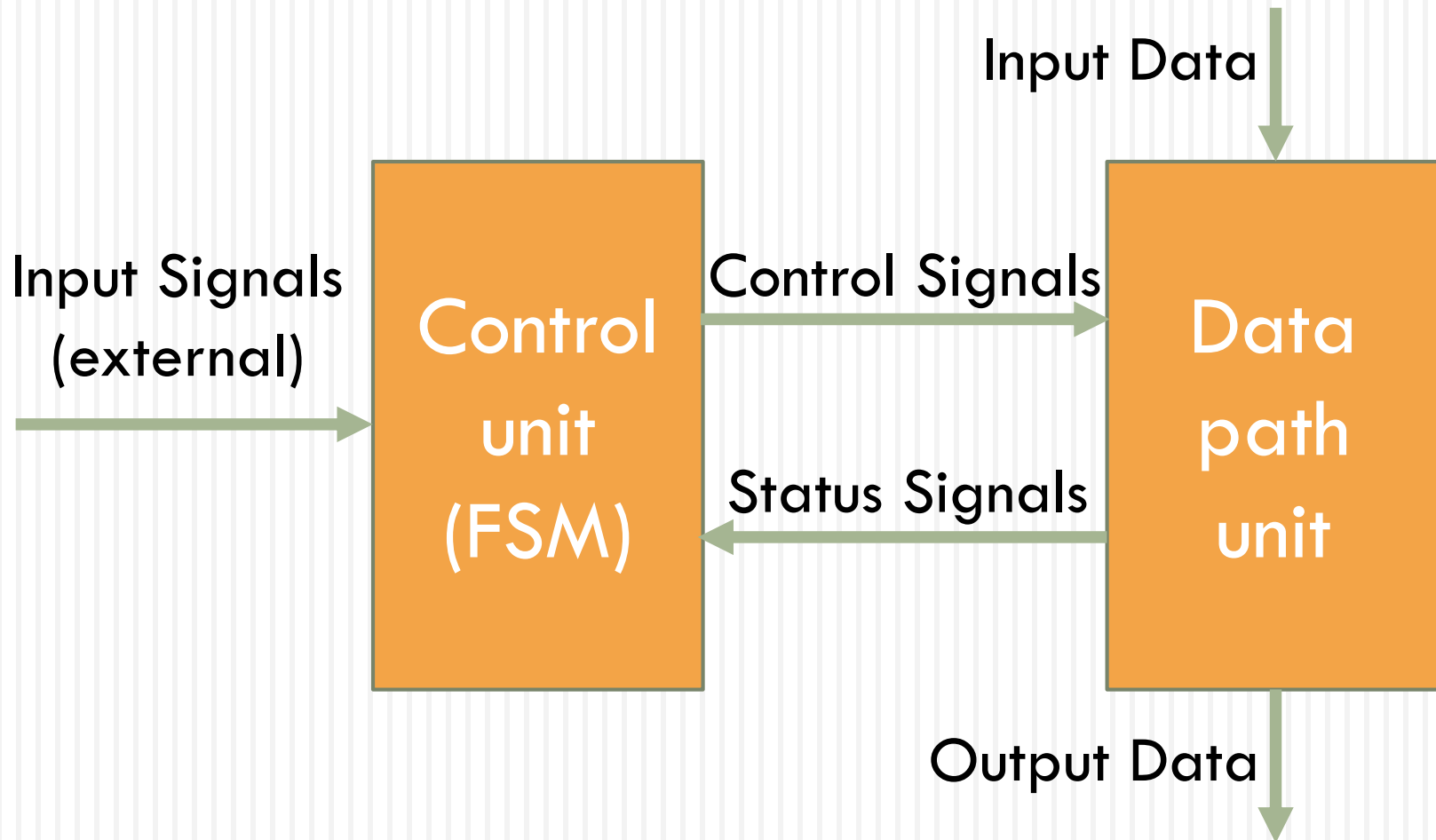

Algorithmic State Machine (ASM) Chart


4

- A flowchart to define digital hardware alg.
- Resembles conventional flowchart
 - ▣ Different interpretation
- Demonstrates
 - ▣ State transitions
 - ▣ Events that occur while going from one state to another
- Three boxes
 - ▣ State box
 - ▣ Decision box
 - ▣ Conditional box

ASM Chart Boxes

5

 
- State box
 - ▣ A state in the control sequence
 - ▣ Contains
 - Register operations
 - Confusing
 - Executed while going to the next state
 - Moore outputs
 - ▣ Can be assigned
 - Name or symbol
 - Binary code



ASM Chart Boxes (Cont.)

6

 - Decision box
 - ▣ Two or more exit paths
 - ▣ Condition to be tested written inside





ASM Chart Boxes (Cont.)

7


□ Conditional box

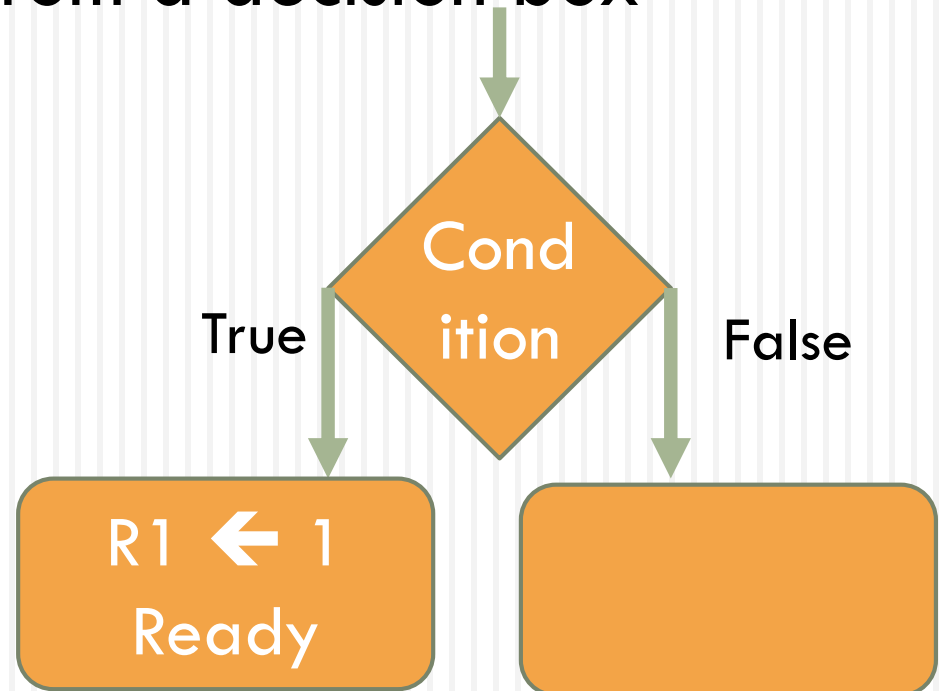- Unique to ASM chart
- Must get its inputs from a decision box
- Written inside
 - Mealy outputs
 - Register operations
 - State transition



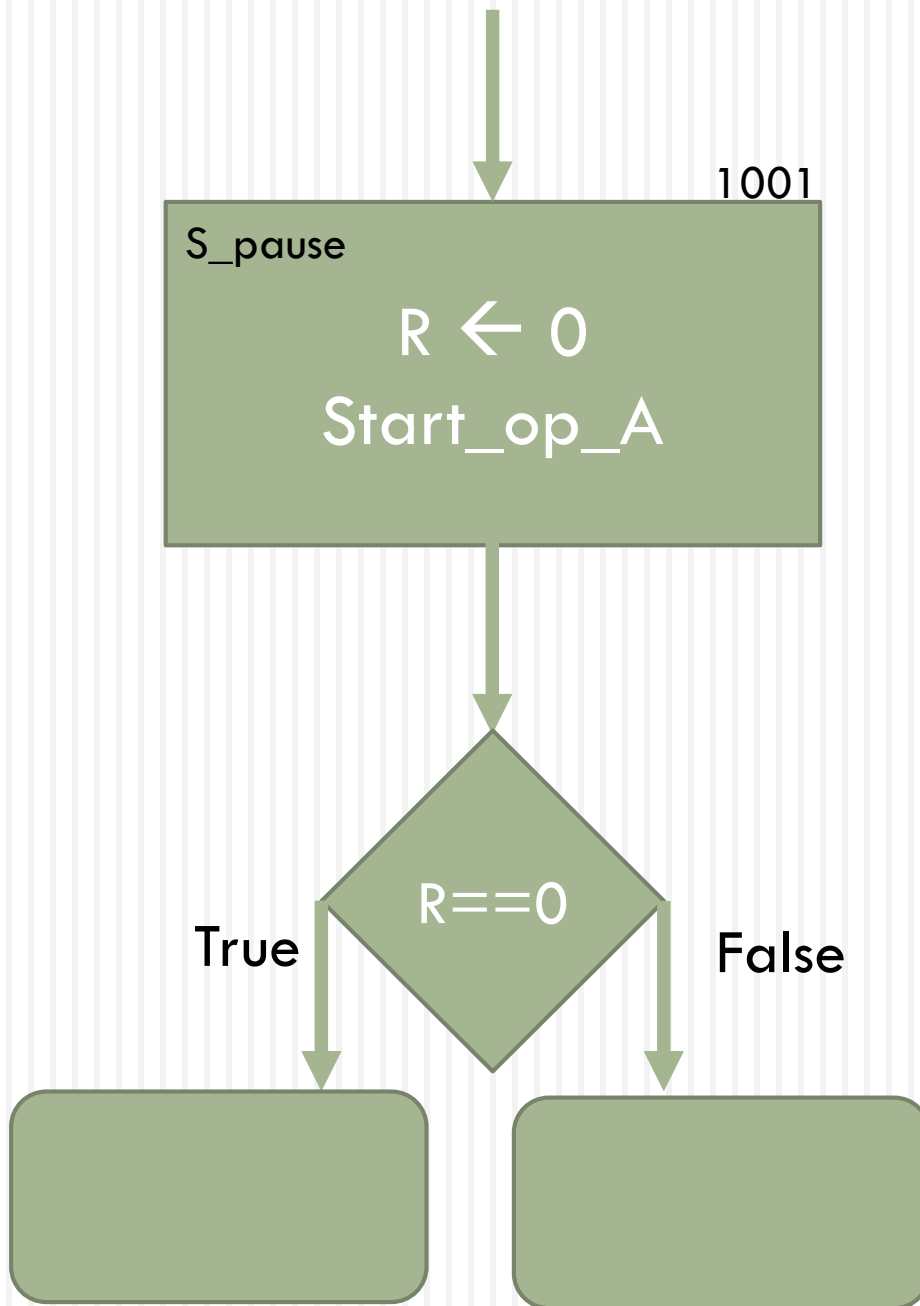

□ Which path is taken?



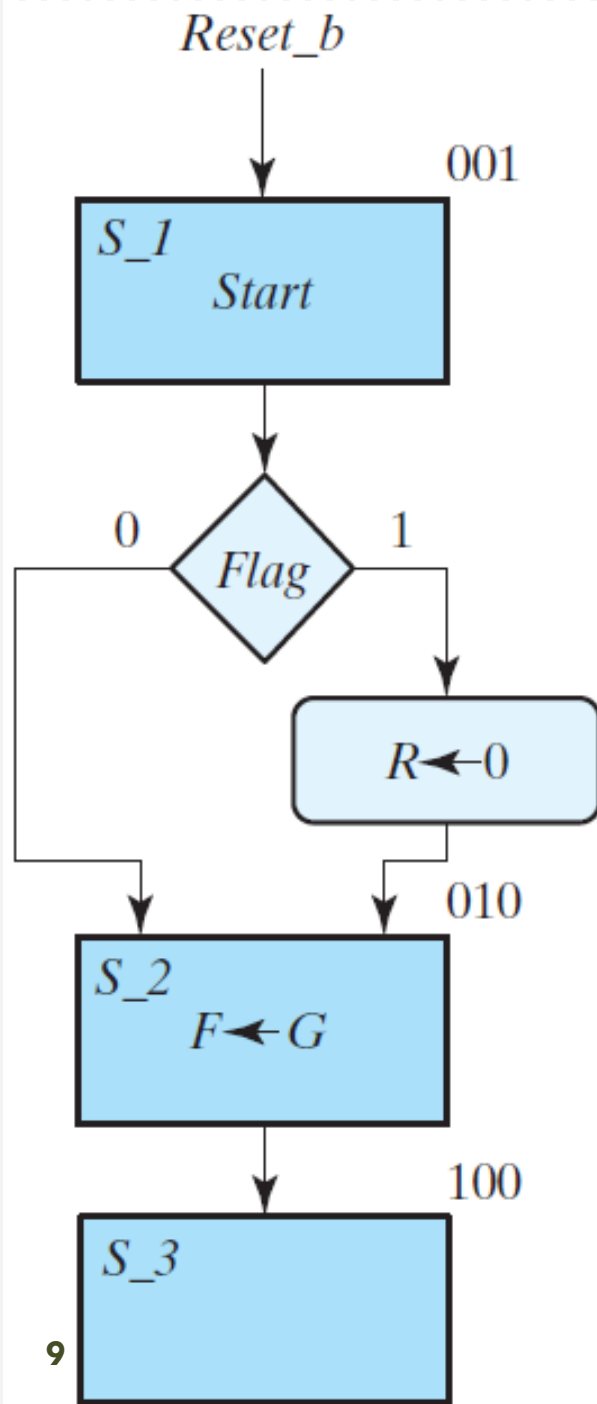


- Control signal 'Start' asserted in S_1
- The value of 'Flag' is checked
 - If $Flag == 1$, R is to be cleared
 - Otherwise, remains unchanged
 - Next state is S_2

ASM Chart (Cont.)

10

□ Some illegal connections

   


ASM Block

11

- One state box & all the decision and conditional boxes connected to the exit path of it
- Only one entrance
- Represents what happens in the system during one clock cycle



ASM Block (Cont.)

12

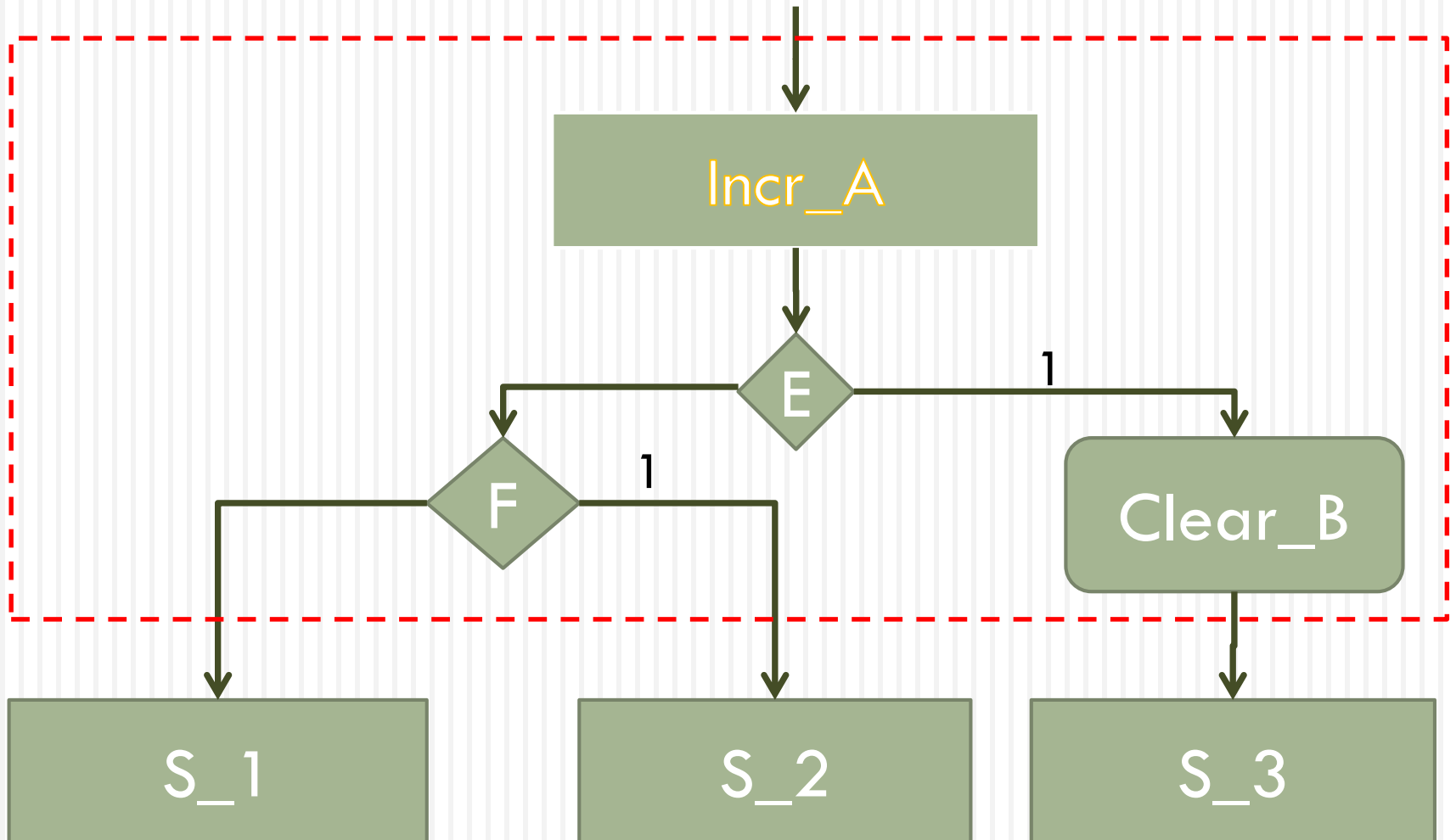

Example: Multiplier

13

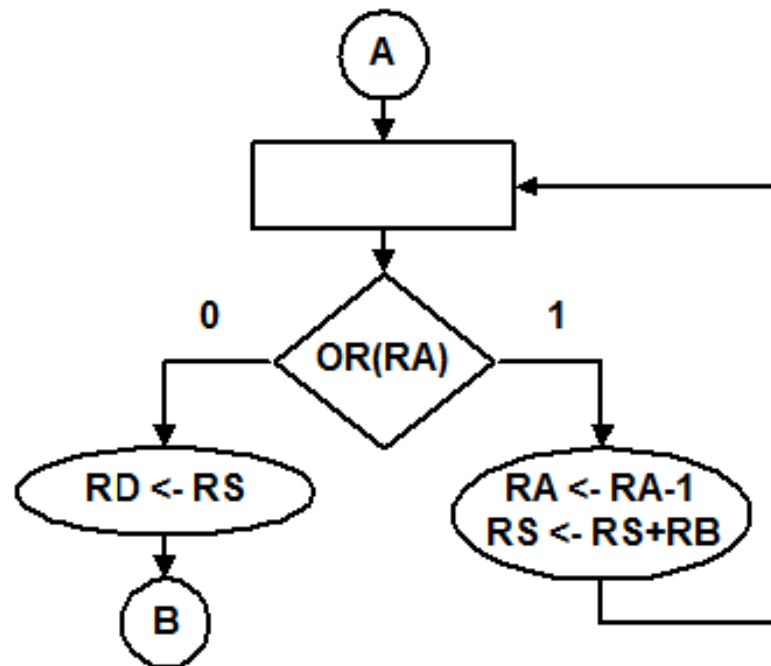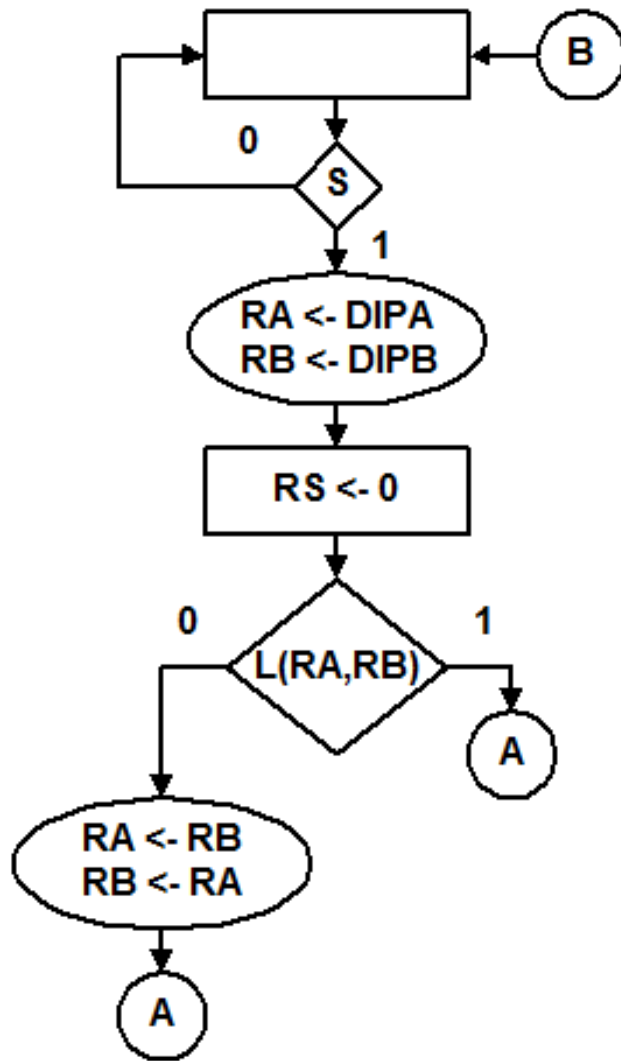

Example (Cont.)

14


□ Datapath

▣ For RA

RA<-DIPA


RA<-RB

RA<-RA-1

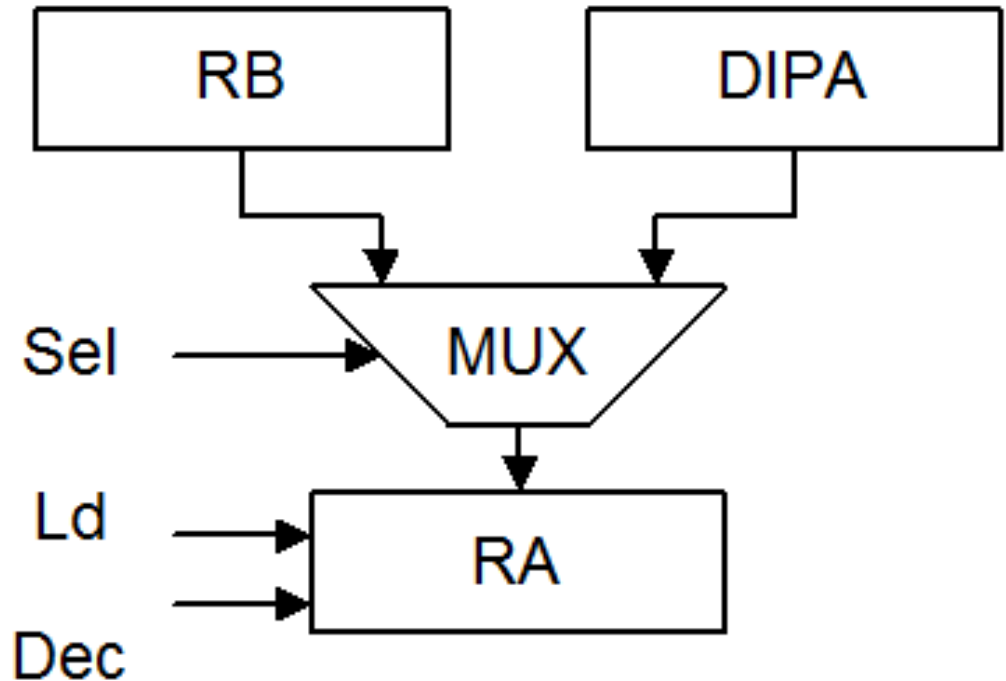

Control Unit (Cont.)

15

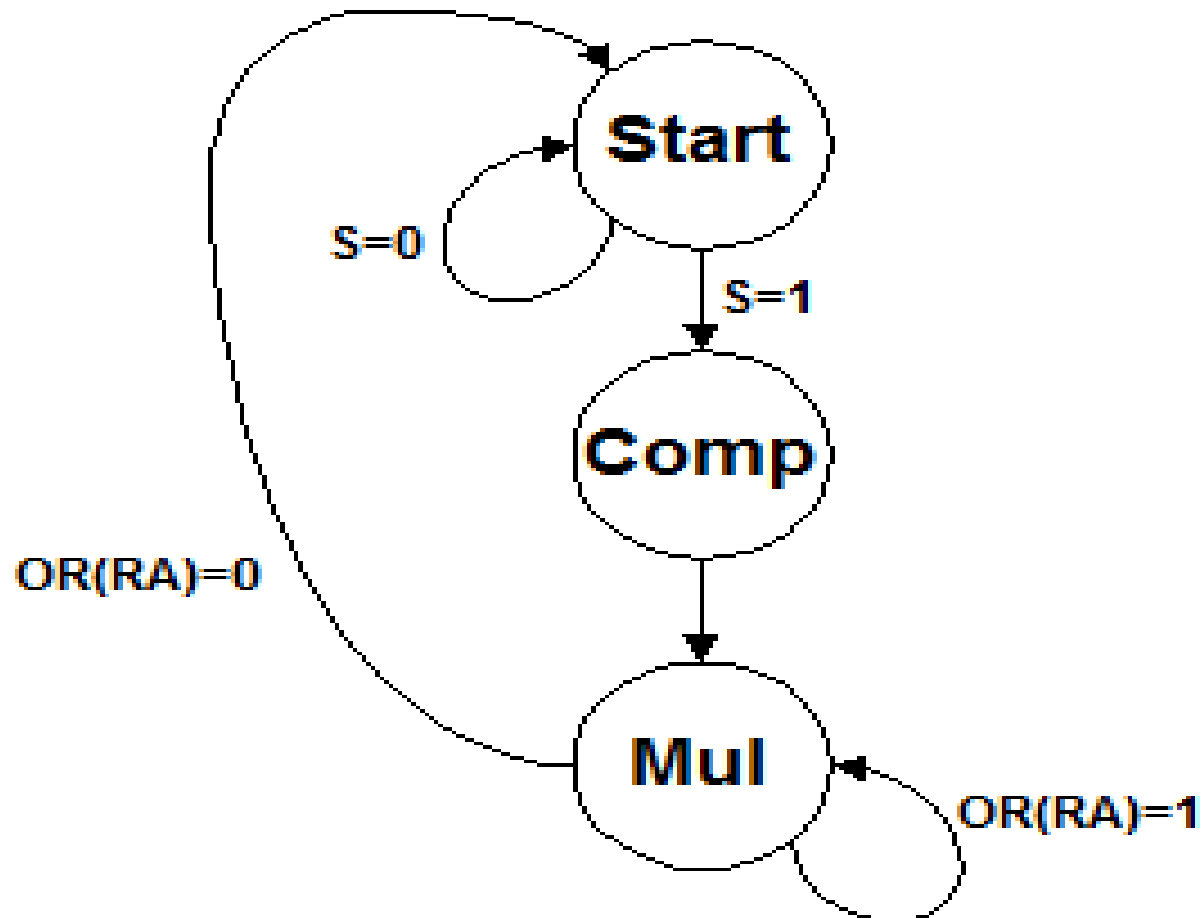

Algorithmic state machine and datapath (ASMD)

16

- To clarify the information displayed by ASM charts
- Differences with ASM
 - ▣ No register operation in state boxes
 - ▣ Edges annotated with register operations
 - ▣ Conditional boxes identify signals controlling register operations

Example

17

□ Specifications

▣ Datapath

- Two JKFFs, i.e., E and F
- One four-bit binary counter, i.e., A[3:0]

▣ *Start*


- Initiation by clearing A and F

▣ At each subsequent clock A incremented

- If $A_2 = 0$, E cleared, count continues
- If $A_2 = 1$, E set
 - If $A_3 = 0$, count continues
 - If $A_3 = 1$, F set, counting stops

Example (Cont.)

18

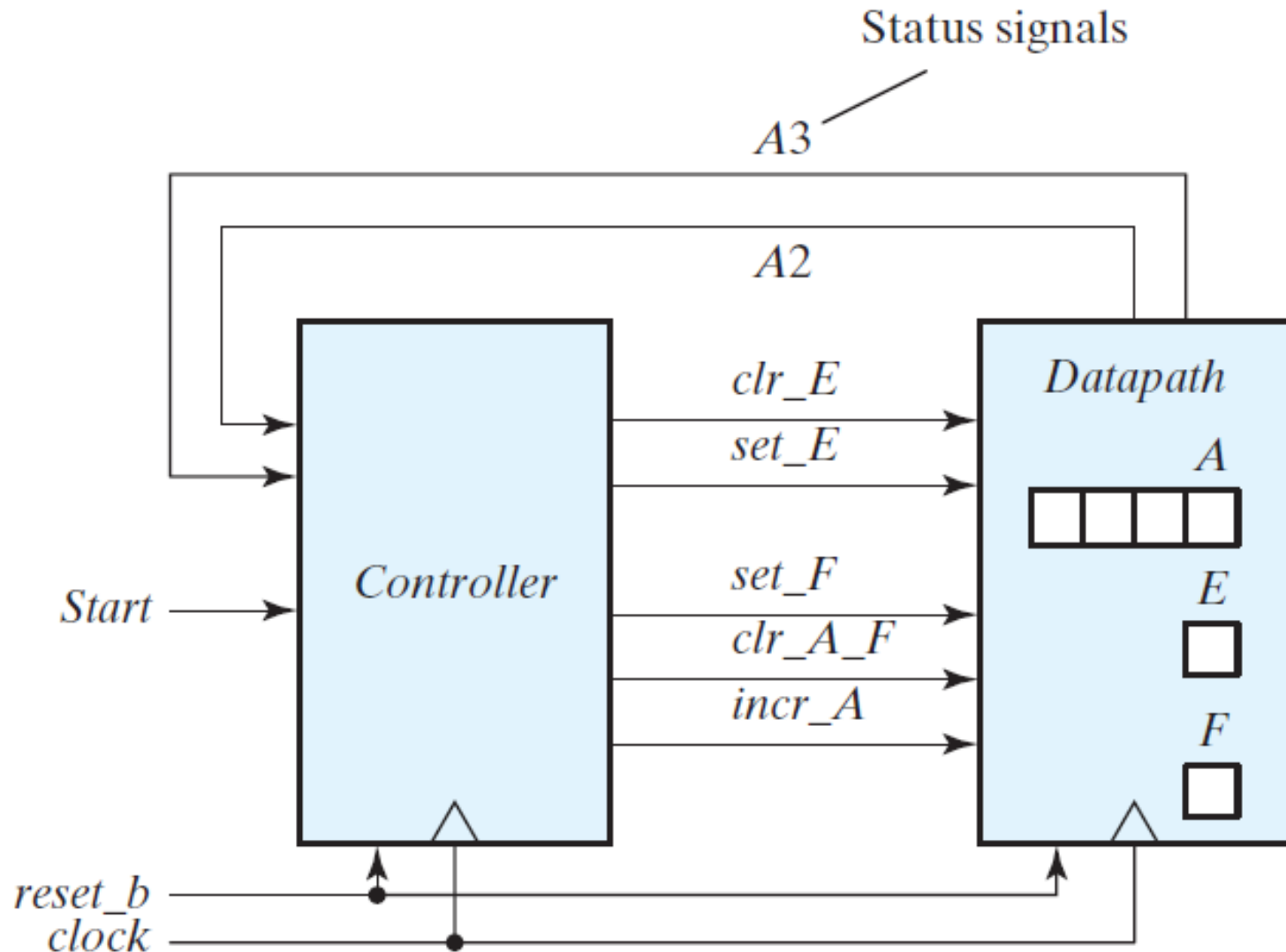

- Synchronous reset
- Register operations annotated on edges leaving

■ A state box


- Occur unconditionally
- Controlled by a Moore-type control signal


■ E.g., $A \leftarrow A + 1$

■ A decision box


- Occur conditionally
- Controlled by a Mealy-type control signal

■ E.g., $E \leftarrow 1$

 

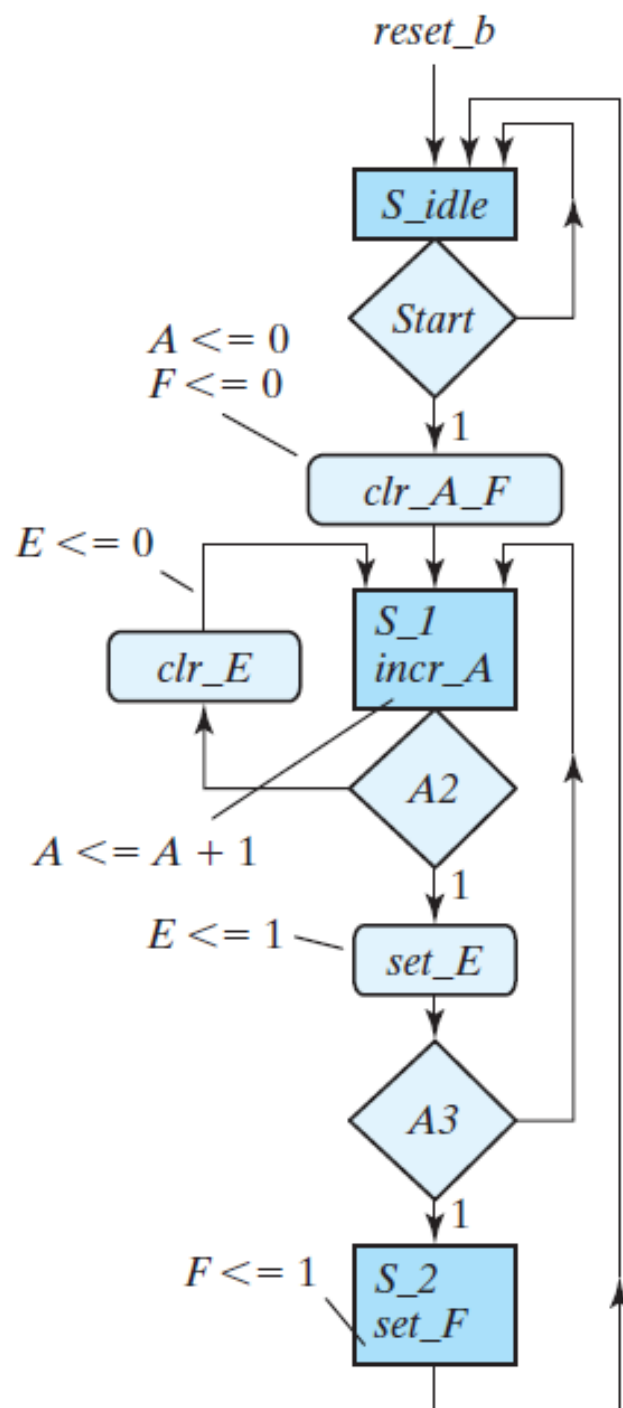


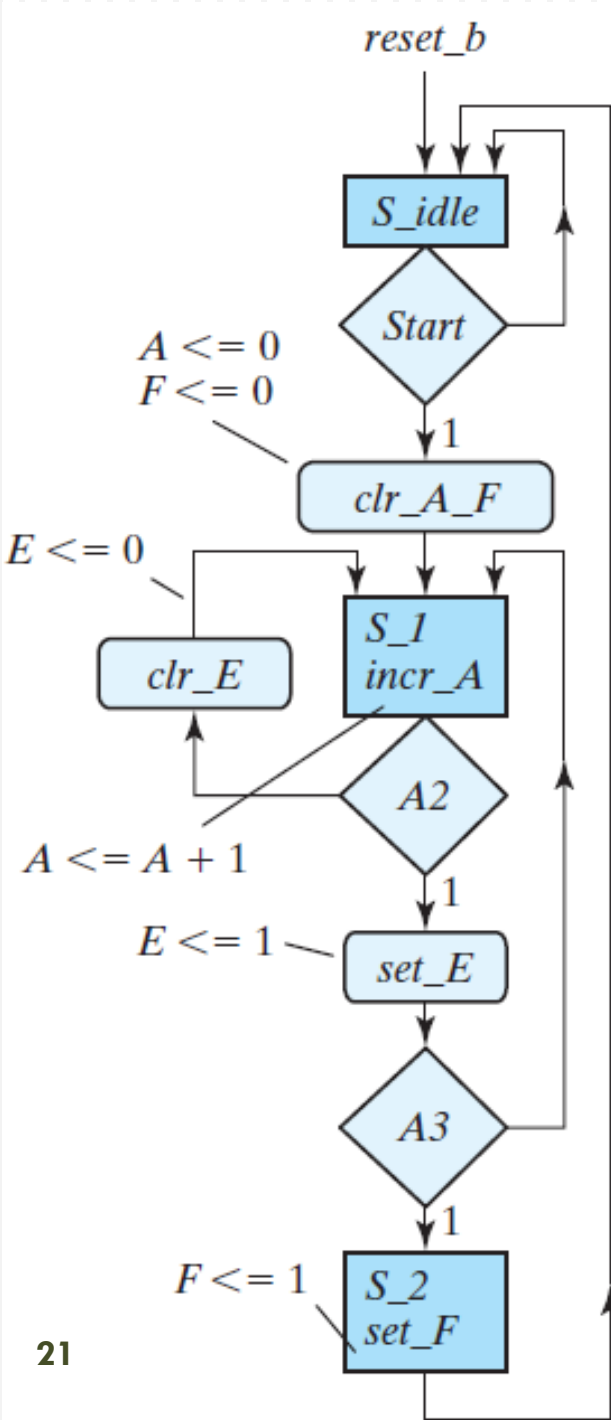
- Asynchronous reset
- Conditional boxes inserted
- Demonstrate control signals in the chart



Sequence of Operations for Design Example

Counter				Flip-Flops		Conditions	State
A ₃	A ₂	A ₁	A ₀	E	F		
0	0	0	0	1	0	A ₂ = 0, A ₃ = 0	S ₁
0	0	0	1	0	0		
0	0	1	0	0	0		
0	0	1	1	0	0		
0	1	0	0	0	0	A ₂ = 1, A ₃ = 0	
0	1	0	1	1	0		
0	1	1	0	1	0		
0	1	1	1	1	0		
1	0	0	0	1	0	A ₂ = 0, A ₃ = 1	
1	0	0	1	0	0		
1	0	1	0	0	0		
1	0	1	1	0	0		
1	1	0	0	0	0	A ₂ = 1, A ₃ = 1	
1	1	0	1	1	0		
1	1	0	1	1	1		S _{idle}

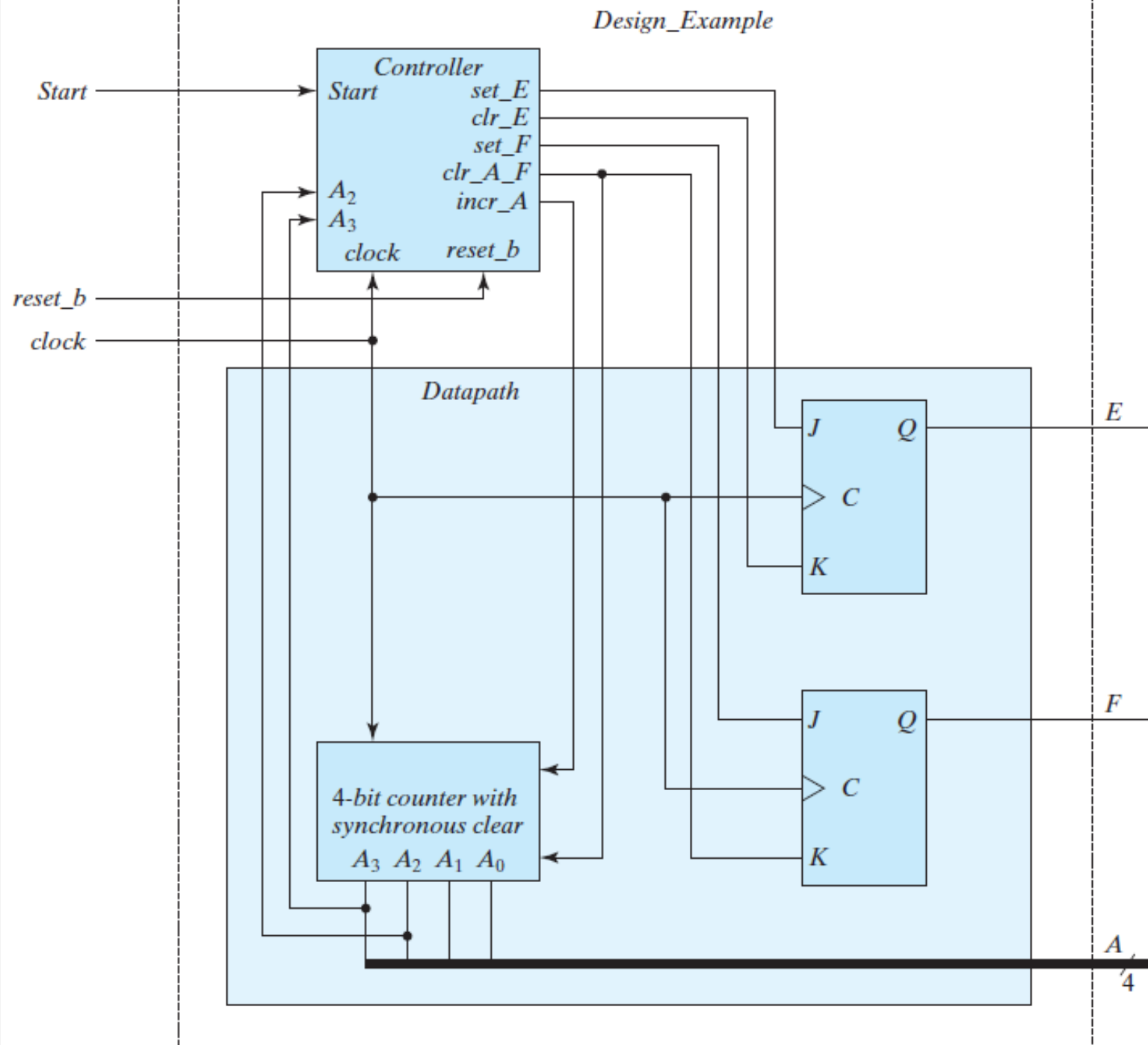

 

(a)

$S_idle \longrightarrow S_1, clr_A_F:$	$A \longleftarrow 0, F \longleftarrow 0$
$S_1 \longrightarrow S_1, incr_A:$	$A \longleftarrow A + 1$
$if (A_2 = 1) \text{ then } set_E:$	$E \longleftarrow 1$
$if (A_2 = 0) \text{ then } clr_E:$	$E \longleftarrow 0$
$S_2 \longrightarrow S_idle, set_F:$	$F \longleftarrow 1$

	Present State		Inputs			Next State		Outputs				
Present-State Symbol	G₁	G₀	Start	A₂	A₃	G₁	G₀	set_E	clr_E	set_F	clr_A_F	incr_A
<i>S_idle</i>	0	0	0	X	X	0	0	0	0	0	0	0
<i>S_idle</i>	0	0	1	X	X	0	1	0	0	0	1	0
<i>S_1</i>	0	1	X	0	X	0	1	0	1	0	0	1
<i>S_1</i>	0	1	X	1	0	0	1	1	0	0	0	1
<i>S_1</i>	0	1	X	1	1	1	1	1	0	0	0	1
<i>S_2</i>	1	1	X	X	X	0	0	0	0	1	0	0

