



Sharif University of Technology
Department of Computer Engineering

Digital System Design

Hierarchical modelling concepts

Siavash Bayat-Sarmadi

Outline

2

- Design methodologies
 - ▣ Top-down
 - ▣ Bottom-up
- Modules
- Module instances
- Components of a simulation

Design Methodology

3

- Top-down

- Define the top level
- Identify the sub-blocks till reaching leaf cells


- Bottom-up

- Identify the available building blocks
- Build bigger till reaching the top-level

Design Methodology (Cont'd)

4


□ 4-bit ripple carry counter

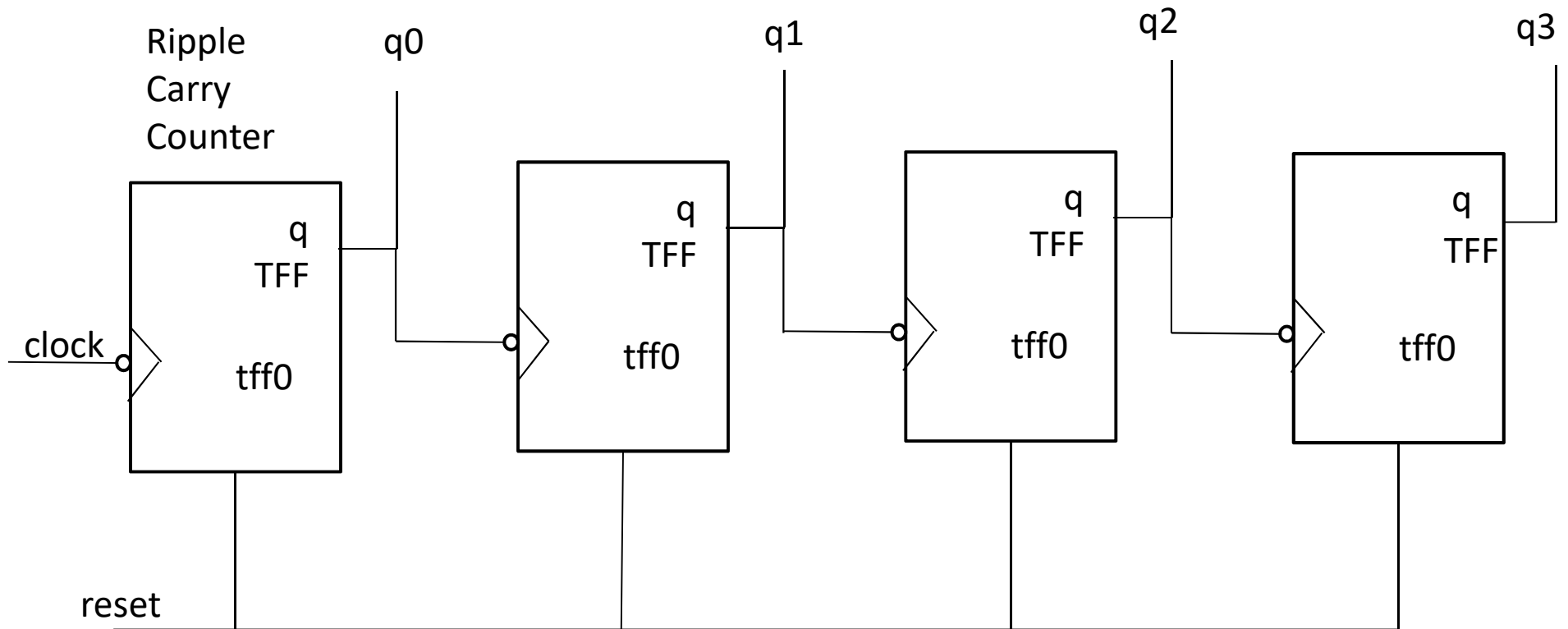

Design Methodology (Cont'd)

5


□ Toggle flip-flop

 

Design Methodology (Cont'd)

6

□ Design hierarchy

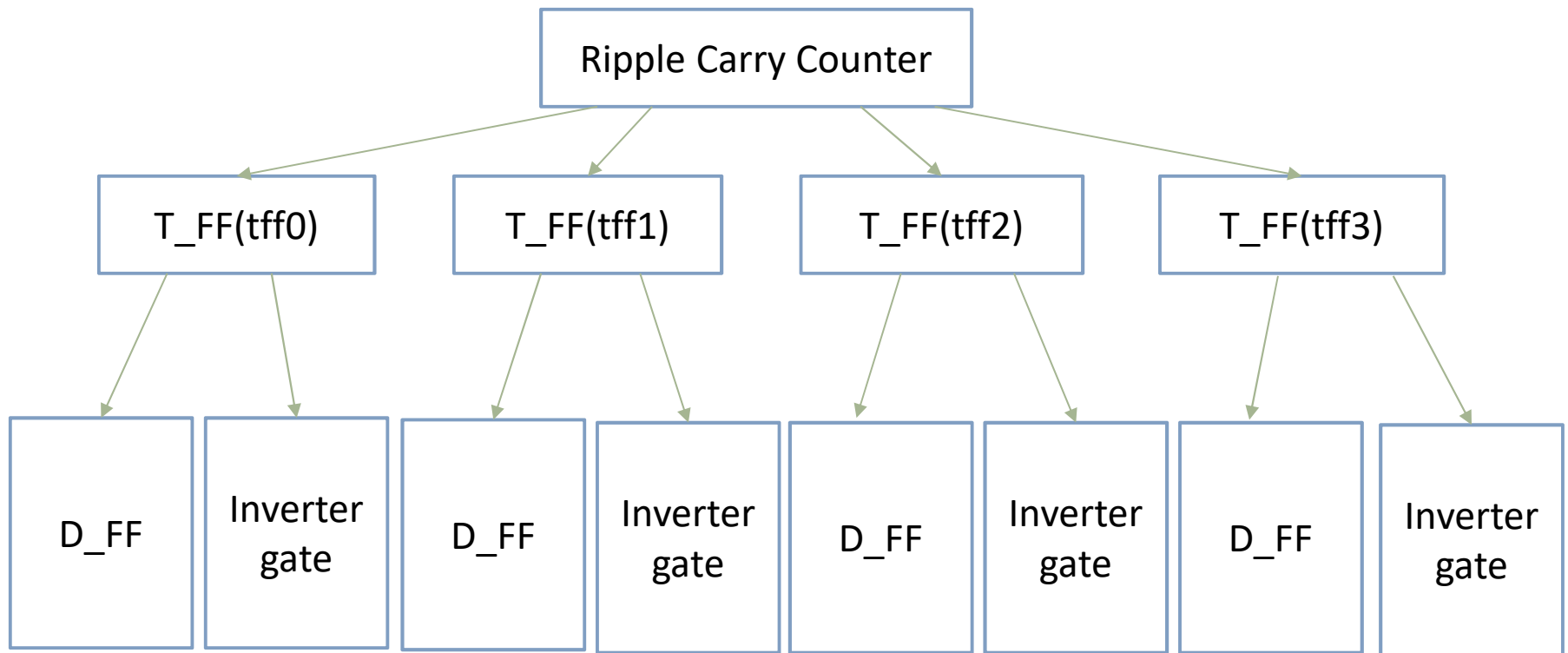

Module

7

- Basic building block in Verilog
- Interacts through its port interface
- Internal implementation hidden to the rest of the design
- Declaration starts with the keyword “module”
- Ends with “endmodule”
- Module definition cannot be nested


Module (Cont'd)

8

Name

Port (terminal) list
 
```
module T_FF (q, clock, reset);  
    ..  
    <functionality of T flip-flop>  
    ..  
endmodule
```



Instance

9

- Modules must be instantiated to be used in the design
- Comparing with C++/Java
 - ▣ Module ~ Class
 - ▣ Instances ~ Objects
- Each instance has its own
 - ▣ Name, variables, parameters, I/O interface, etc.

Instances (Cont'd)

10


//top-level

module ripple_carry_counter(q, clk, reset);

output [3:0] q;

input clk, reset;

Module
name

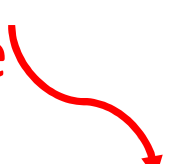

Instance name



T_FF tff0 (q[0], clk, reset);

T_FF tff1 (q[1], q[0], reset);

T_FF tff2 (q[2], q[1], reset);

T_FF tff3 (q[3], q[2], reset);


endmodule

Components of a Simulation

11

□ Test bench

 
- ▣ Testing functionality of the design
 - By applying stimulus
 - And checking the results




Components of a Simulation (Cont'd)

12

 - Test bench instantiating the design block



 - A dummy top-level module instantiating both



Components of a Simulation (Cont'd)

13

```
module stimulus;
  reg clk;
  reg reset
  wire [3:0] q;

  ripple_carry_counter
  r1 (q, clk , reset);

  initial
    clk = 1'b0;
```

```
always
  #5 clk = ~clk;
initial
begin
  reset = 1;
  #15 reset = 0;
  #180 reset = 1;
  #10 reset = 0;
end
```

Components of a Simulation (Cont'd)

14

