



Sharif University of Technology
Department of Computer Engineering

Digital System Design

Modules and ports

Siavash Bayat-Sarmadi

Outline

2

- Components of a Verilog module, i.e. name, port list, etc.
- Port connection rules
- Connecting port by ordered list and name
- Hierarchical name

Components of a module

3

- Previously discussed how to
 - ▣ Define
 - ▣ Instantiate
- Currently
 - ▣ Module internals

Components of a module

4

Module name,

Port List, port declaration (if ports present)

Parameters (optional)

Declaration of **wires** , **regs** and other variable

data flow statement (**assign**)

Instantiate of lower level modules



Always and **initial** blocks: all behavioral statements go in these blocks.

Task and **function**


Endmodule statement

Components of a module

5

Name  **module**  **Port (terminal) list** adder (sum, cout, a, b);

output [1:0] sum;
output cout;
input [1:0] a, b;

 **Port declaration**

parameter delay=1; **Parameters**

...

endmodule

Components of a module (cont'd)

6

```
module adder (sum, cout, a, b);
```


...

Declaration of wires
and regs and other variables

```
wire carry0, carry1;
```

...

```
endmodule
```

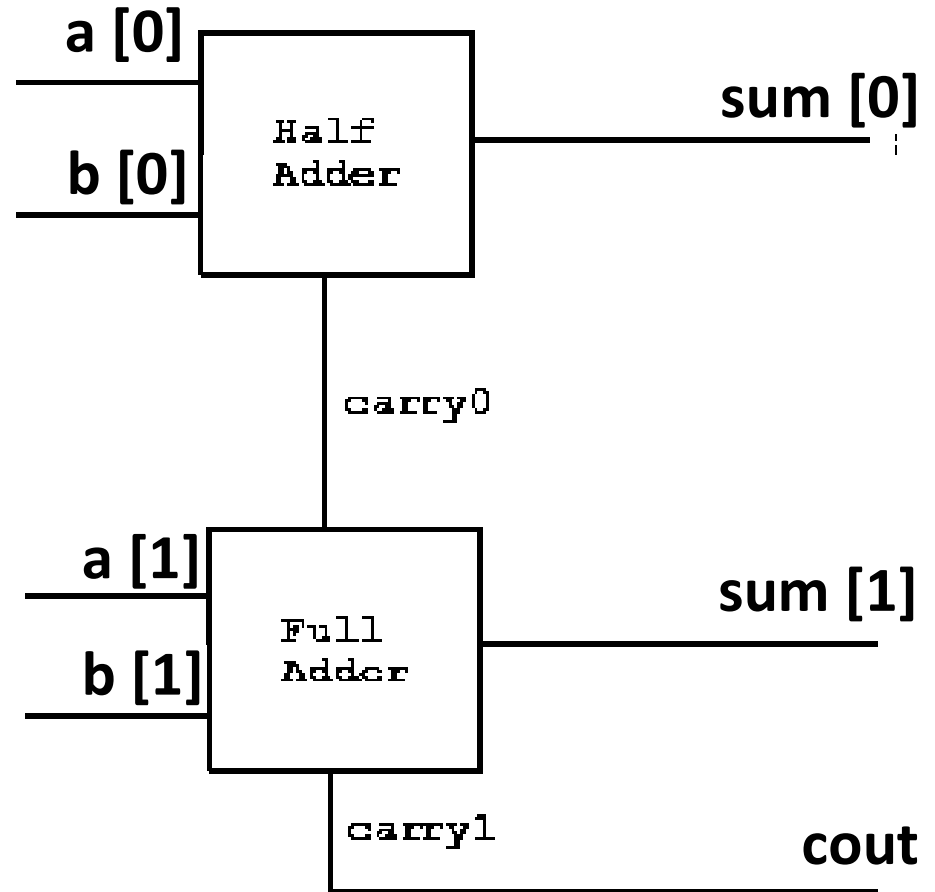

Components of a module (cont'd)

7

- Default type for port
 - ▣ wire
 - ▣ If not specified
- Port list and declaration can be mixed
 - ▣ **output wire** [1:0] sum;
 - ▣ **module** adder (**output** [1:0] sum, ...
 - ▣ **module** adder (**output wire** [1:0] sum, ...

Components of a module (cont'd)

8

```
module adder (sum, cout, a, b);
```

```
...
```

```
...
```

Instantiation of lower
modules

```
halfAdder ha (sum[0], carry0, a[0], b[0]);
```

```
fullAdder fa (sum[1], cout, a[1], b[1], carry0);
```

```
endmodule
```


Components of a module (cont'd)

9

- Dataflow statements
 - ▣ **assign**
- Behavioral blocks
 - ▣ **always**
 - ▣ **initial**
- **tasks** and **functions**

Ports

10

- Module inputs and outputs
- Optional for modules
 - ▣ Top-level module doesn't have ports
- Port types
 - ▣ **input**
 - ▣ **output**
 - ▣ **inout**
 - Be extra-careful with this type

Ports (cont'd)

11

- Width matching
 - ▣ Internal and external connections can have different sizes
 - ▣ A warning will be issued by synthesizer
- Unconnected ports
 - ▣ `fulladd4 fa0(SUM, , A, B, C_IN);`

Ports (cont'd)


12

- Connecting to external signals (cannot be mixed):
 - ▣ By ordered list
 - ▣ by name
- Example: **module** adder (sum, cout, a, b);
 - ▣ adder adderInstance1 (s, c, a, b);
 - ▣ adder adderInstance2 (.sum (s), .cout (c), .a (a), ...

Port Connection Rules

13

Note when instantiating
a module

 

inout

net

net

Note when declaring
a module

input

output



net


reg / net

net

Hierarchical Names

14

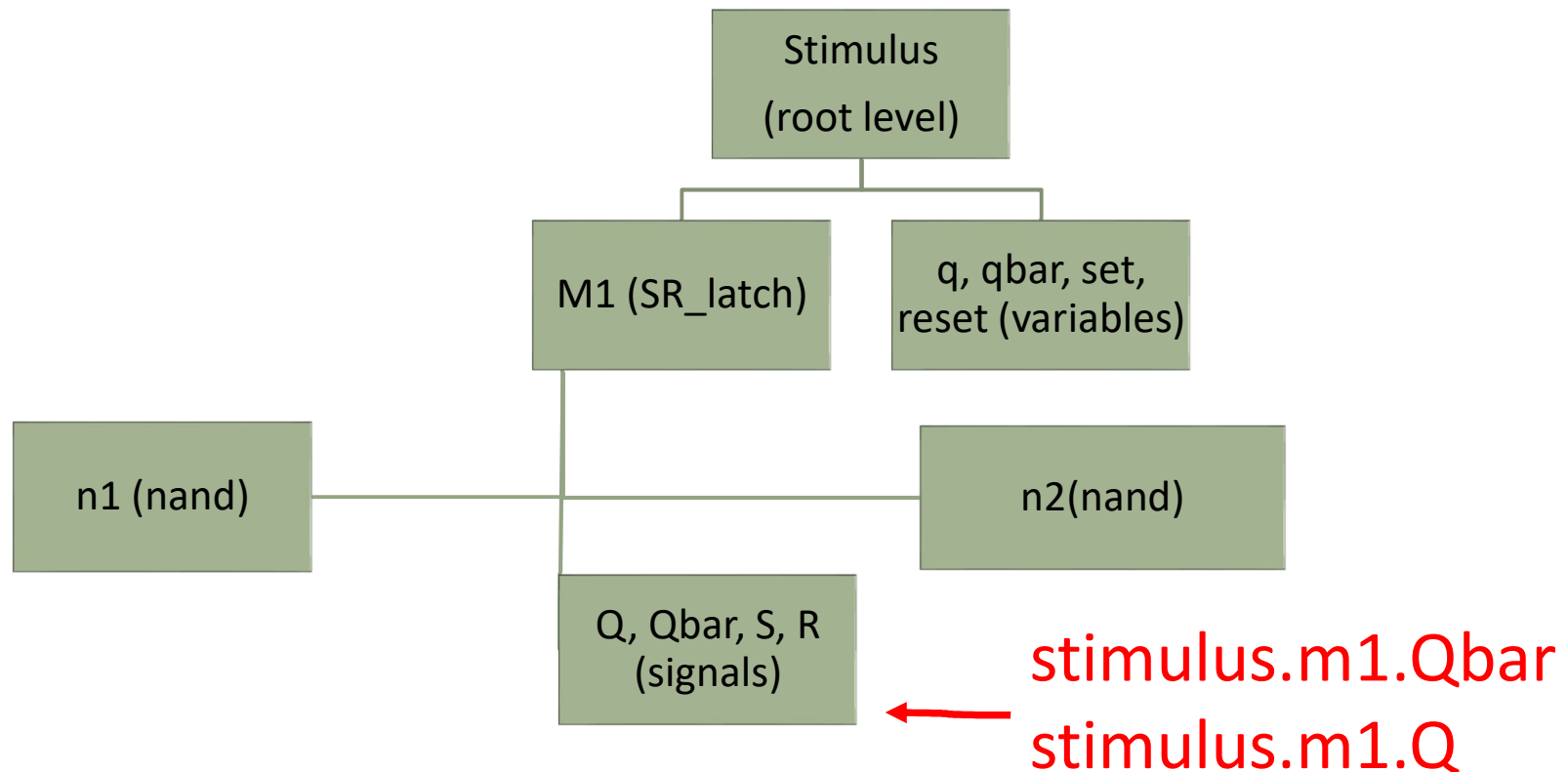- Every identifier a unique name
- \$display ("%m")



Part-2

16-bit RISC Processor

Ripple Carry Adder

Outline

16

- Introduction to module and port
- Design Ripple carry adder
- Review Common Mistake
- Handle Errors

4-bit Ripple Carry Adder

17

