



Sharif University of Technology
Department of Computer Engineering


Digital System Design

Metastability & Clock Domain Crossing (CDC)


Siavash Bayat-Sarmadi

Introduction

□ Flip-flop setup & hold times

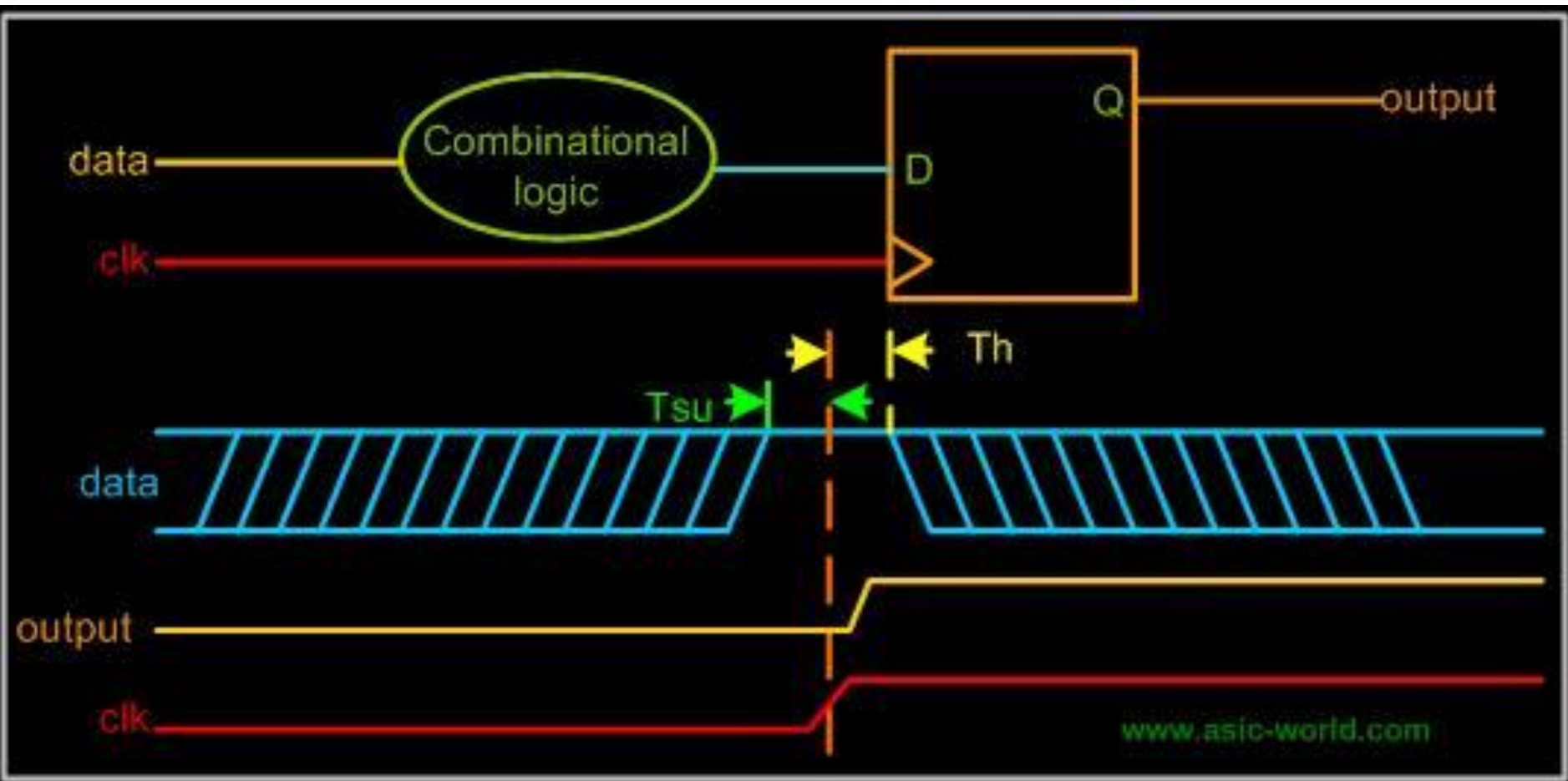

Metastability

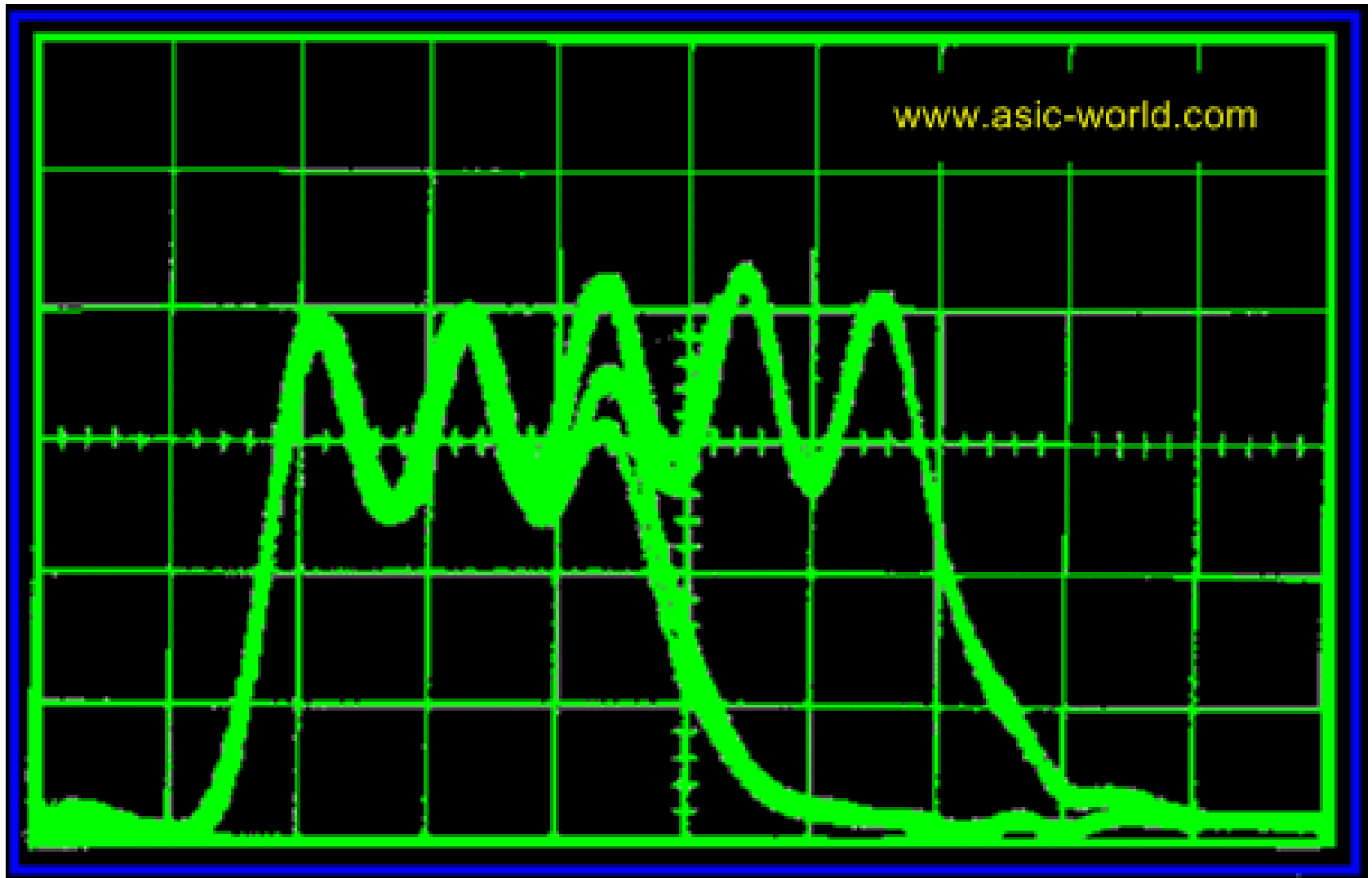

Metastable State

- A state for a flip-flop with unpredictable output
 - ▣ Quasi stable state
 - ▣ Output oscillating between 0 and 1
 - ▣ Taking longer time to settle down than usual
 - ▣ As an outcome of timing violations
 - Setup or hold issues
 - E.g., d/reset and clock changing at the same time

What are the causes? (1)

- Asynchronous input signal that can change at any time
 - ▣ Not in designer's control
- Too much clock skew
 - ▣ Rise and fall time more than the tolerable values

What are the causes? (2)

6

- Data input changing in the critical window
 - ▣ Critical window = setup + hold window
 - ▣ As an outcome of long combinational delay
- When interfacing two clock domains
 - ▣ Different frequencies
 - ▣ Same frequency, different phases
 - ▣ Discussed later in this lecture

How to tolerate? (1)



- Long enough clock period
 - ▣ For the quasi state to settle down
 - ▣ And for the follow-up path to the next flip-flop
 - ▣ Performance degradation, not always acceptable
- Metastable-hardened flip-flops
 - ▣ Reduced setup and hold times as much as possible

How to tolerate? (2)

SYNC Flip Flop

◆ SYNC Flip Flops are available in some ASIC libraries

  
- Better MTBF characteristics due to high gain in the feedback path
- Very large (5x regular FF) and very high power



Interfacing Two Clock Domains

Introduction

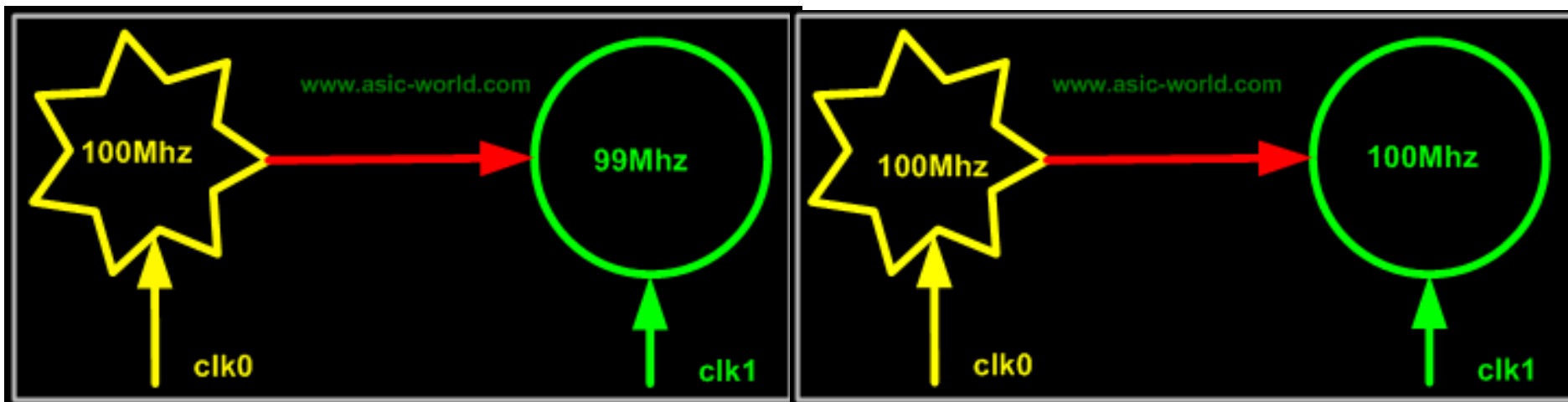
- Any two systems considered asynchronous to each other when working at
 - ▣ Different frequencies
 - ▣ Same frequency, but different phases



How to do data transfer?


11

 - Handshake signaling
 - ▣ System A sends data to system B based on
 - the handshake signals
 - req
 - Ack
- Asynchronous FIFO
 - ▣ Two Clocks
 - ▣ Two data interfaces



Handshake Signaling (1)

 
- Transmitter asserts req
 - ▣ asking the receiver to accept the data on the data bus
- Receiver asserts ack
 - ▣ asserting that it has accepted the data



Handshake Signaling (2)

13

 
- Asynchronous input to the receiver
 - ▣ Setup/hold time violations possible
 - Double or triple stage synchronizers
 - Req
 - necessary



Handshake Signaling (3)

14

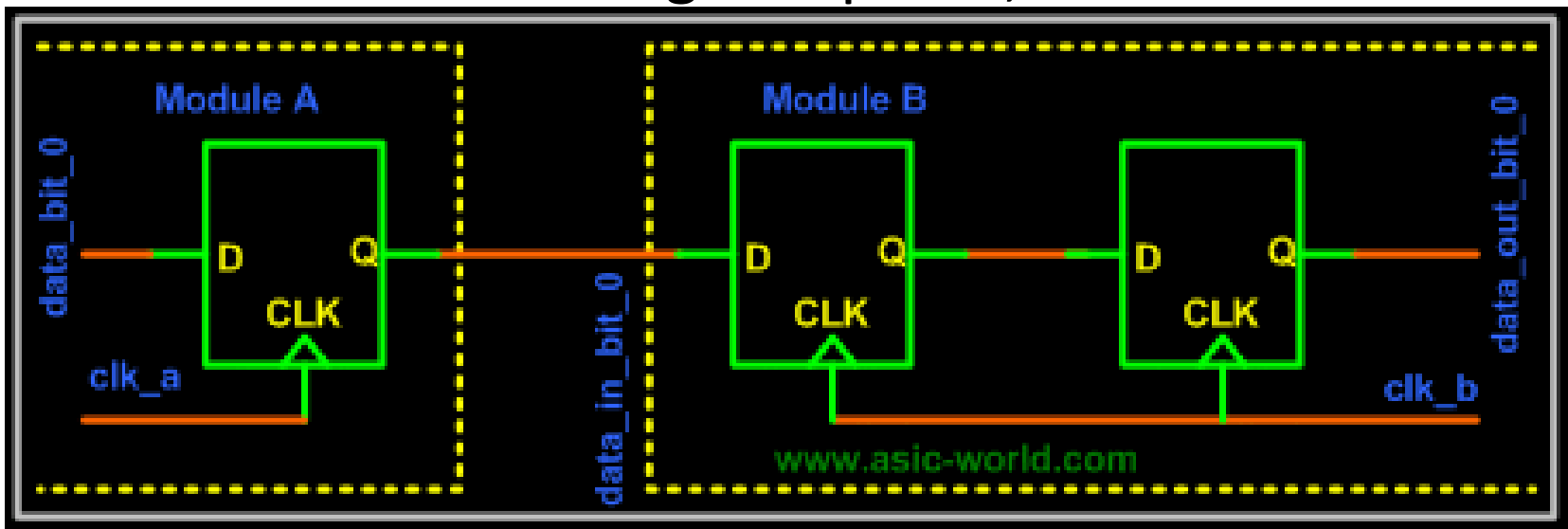
- Asynchronous input to the receiver
 - ▣ Setup/hold time violations possible
 - Double or triple stage synchronizers
 - Data
 - Lots of logic required, usu. not used



Handshake Signaling (4)

15

 - A lot of clock cycles wasted handshaking
 - ▣ Use Asynchronous FIFO



- ▣ High frequency input

Asynchronous FIFO (1)

16

- Two interfaces
 - ▣ One for writing the data into the FIFO
 - ▣ One for reading the data out
- Two clocks
 - ▣ One for writing
 - ▣ One for reading

Asynchronous FIFO (2)

17

- FIFO full
 - ▣ Used by system A
 - ▣ Driven by write clock (system A clock)
- FIFO empty
 - ▣ Used by system B
 - ▣ Driven by read clock (system B clock)

Asynchronous FIFO (3)

18

- Compared with handshaking
 - ▣ Higher performance
 - ▣ More resources

